


Homework 2

- Design two separate combinational circuits at the gate level for the middle and bottom segments of a seven-segment display. Make sure your design uses the minimum number of logic gates with minimum number of inputs. The 4-bit inputs are (x_3, x_2, x_1, x_0) , and the single output is the signal for lighting the desired segment, which is 1 when needed for displaying the decimal digit (0–9) represented by the binary input, or 0 otherwise. Treat the combinations of inputs that represent 10–15 as “don’t cares.”
- Assume you need a 64-to-1 multiplexer controlled by six select signals A through F, i.e., a binary number ABCDEF specifies the index of the input to be sent to the output. However, as we assume a logic gate can not have more than eight inputs; such a MUX is not directly available.

- How would you build this 64-to-1 MUX using 4-to-1 MUXs? Label clearly in your design how the signals A through F are used in your design.
- Assume you have only eight 8-to-1 MUXs available. How would you build the 64-to-1 MUX using these MUXs and minimum additional logic gates (NOT, AND and OR only)? Again, show how the six select signals are used in your design.

Hint: in your design, you can assume each circuit has an $\overline{\text{enable}}$ input that, when set to 0, enables the circuit to do whatever it is supposed to do, but when set to 1, disables the circuit so that the output is always 0.

 - Implement the three functions $f(A, B, C) = \Sigma(1, 2, 4, 6, 7)$, $g(A, B, C) = \Sigma(0, 2, 3, 5)$, and $h(A, B, C) = \Sigma(2, 3, 4, 6)$ by disconnecting (marking by “x”) all necessary links in the AND and OR arrays in the PLA given in the following figure.




- A full adder was discussed and simulated in Lab 1. Now consider a 1-bit full adder/subtractor. The two input bits and are to be operated on, under the control of a signal k ($k = 0$ for addition; $k = 1$ for subtraction). Another input is for either the carry or borrow from the lower bit. The outputs include the result r (sum or difference) and $cout$ for carry or borrow to the next higher bit.


- Design this 4-input 2-output circuit and implement it at the logic gate level. Make sure to minimize the hardware as much as possible.
 - How would you implement this circuit with two 8-input MUXs and minimal number of inverters?
- Hint: Try the example $1101000110 - 011001010 = ?$ to help yourself figure out how to do binary

subtraction. If you are still not sure how to subtract, try a decimal subtraction such as $123 - 89 = ?$.

- Design a comparator circuit that takes two 4-bit words, $a_3a_2a_1a_0$ and $b_3b_2b_1b_0$, as inputs, and generates one output f that is 1 if the two words are identical, i.e. $a_i = b_i$, $i = 0, 1, 2, 3$. Note that there are eight input variables and $2^8 = 256$ minterms in the truth table. Obviously K-map simplification (containing 256 squares) cannot be used. (Hint: consider XNOR, which is a 1-bit comparator.)
- Design a left/right shifter that takes a word of four bits $D_3D_2D_1D_0$ as input, and generates as output a word also of four bits $S_3S_2S_1S_0$, which is a shifted version of the input. When a control signal k is equal to 1, the input word is shifted to the right by 1 bit to become the output, i.e. $S_i = D_{i+1}$, for $i = 0, 1, 2$, and $S_3 = D_0$ (right rotation). When $k = 0$, the input word is shifted to the left by 1 bit, so $S_i = D_{i-1}$, for $i = 1, 2, 3$, and $S_0 = D_3$ (left rotation). Note that the truth table of this circuit with five $(4 + 1)$ inputs has $2^5 = 32$ minterms, and the K-map simplification method would be very difficult to use.

 

 - Design the interface circuit between computer 1 and computer 2 for transmitting any of the four letters A, B, C and D, which are coded by three bits x_3, x_2, x_1 in computer 1 but 2 bits y_2, y_1 in computer 2, as shown below. Note that all x s in the table mean "don't care" (either 1 or 0); i.e., the letter A is coded in computer 1 by 010, 011 or 100.



	A	B	C	D
x_1	0	1	1	0
x_2	1	0	1	0
x_3	x	0	x	1
y_1	0	0	1	1
y_2	0	1	0	1

Give the gate level implementation of the interface circuit. Can you use only five logic gates (excluding NOT gates) for the circuit to generate both y_2 and y_1 ?