 


The Flipflops

The Basic Memory Cell: Latches


Feedback is the key to having memory capability. Here is the simplest circuit that can remember one bit of information:



Two types of latches can be built by using either NAND or NOR gates. First recall the basic logic of these gates:


A	B	$(AB)'$	$(A + B)'$
0	0	1	1
0	1	1	0
1	0	1	0
1	1	0	0

NAND latch

 

set	reset	Q_{t+1}	\overline{Q}_{t+1}	
0	0	1	1	
0	1	1	0	(set or preset)
1	0	0	1	(clear or reset)
1	1	Q_t	\overline{Q}_t	(no change: $Q_t = Q_{t+1}$)

NOR latch

 


set	reset	Q_{t+1}	\overline{Q}_{t+1}	
0	0	Q_t	\overline{Q}_t	(no change: $Q_t = Q_{t+1}$)
0	1	0	1	(reset)
1	0	1	0	(set)
1	1	0	0	

Clocked Latches: Flipflops

RS-Flipflop (Set-Reset):

Clock	S	R	\overline{set}	\overline{reset}	Q_{t+1}	\overline{Q}_{t+1}	
0	x	x	1	1	Q_t	\overline{Q}_t	(no change)
1	0	0	1	1	Q_t	\overline{Q}_t	(no change)
1	0	1	1	0	0	1	(reset)
1	1	0	0	1	1	0	(set)
1	1	1	0	0	1	1	(not allowed *)

 


S and R are not allowed to be 1 at the same time, as the states of Q and \overline{Q} are unpredictable when the clock becomes 0.

D-Flipflop (Delay)

To avoid the undesirable state $S = R = 1$ in an RS-FF, we let $R = S'$ and rename S as D. Now only the middle two states in the above RS-FF remain, and the resulting circuit is a D-flipflop:


Clock	D	\overline{set}	\overline{reset}	Q_{t+1}	\overline{Q}_{t+1}	
0	x	1	1	Q_t	\overline{Q}_t	(no change)
1	0	0	1	0	1	(reset)
1	1	1	0	1	0	(set)

 

JK-Flipflop


Feedback can be used as another way to avoid the unpredictable state in an RS-FF. The output Q and \bar{Q} are sent back to the set and reset side, respectively, and the S and R inputs are renamed as J and K. Now Q and \bar{Q} are guaranteed to be always opposite to each other.

Clock	J	K	Q_t	\bar{Q}_t	\overline{set}	\overline{reset}	Q_{t+1}	\bar{Q}_{t+1}	
0	x	x	x	x	1	1	Q	\bar{Q}	(no change)
1	0	0	x	x	1	1	Q	\bar{Q}	(no change)
1	0	1	0	1	1	1	0	1	(no change)
1	0	1	1	0	1	0	0	1	(reset)
1	1	0	0	1	0	1	1	0	(set)
1	1	0	1	0	1	1	1	0	(no change)
1	1	1	0	1	0	1	1	0	(set)
1	1	1	1	0	1	0	0	1	(reset)

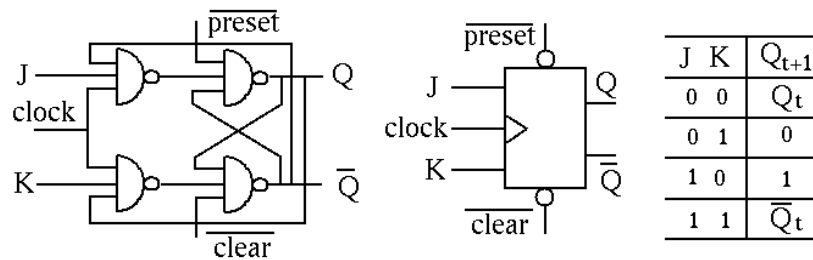

T-Flipflop (Toggle)

 If the J and K inputs are tied together and renamed as T (for toggle), only the first and last states of JK-FF remain, and the FF becomes a toggle FF:



Summary

The different types of Flipflops (RS, JK, D and T) can also be described by their excitation table, as shown below. The left side shows the desired transition from $Q(t)$ to $Q(t+1)$, and the right side gives the triggering signals needed for the transitions in various types of FFs.

Desired transition		Triggering signal needed					
$Q(t)$	$Q(t+1)$	S	R	J	K	D	T
0	0	0	x	0	x	0	0
0	1	1	0	1	x	1	1
1	0	0	1	x	1	0	1
1	1	x	0	x	0	1	0